

11. Graphs all have the same shapes as the simulation graphs
12. Increasing the capacitance will smooth out the output voltage while decreasing the capacitance will have the opposite effect
13. Increasing R_1 would decrease the amplitude of the output voltage. The ideal R_1 would be whatever gives the desired output voltage.
14. Decreasing R_2 would also decrease the amplitude of the output voltage.