



University Of Texas At Austin	
Schematic Name: Lab3 Alarm Clock	
Name(s): Stephen Hall and Razik Ahmed	
Date: Sept. 10, 2010	Semester: Fall 2010

All resistors are 1/4 watt 5% carbon composition.
 C1 is ceramic Z5U
 Switches are B3F-1052 Digikay SW405-ND
 Red LEDs, T1 3/4, 20mA Digikay 160-1087-ND
 Yellow LEDs, T1 3/4, 20mA Digikay 160-1088-ND
 Green LEDs, T1 3/4, 20mA Digikay 160-1089-ND
 Slide pot, Alpha RA3008F-10-20D1-B54 Mouser# 312-9100F-50K